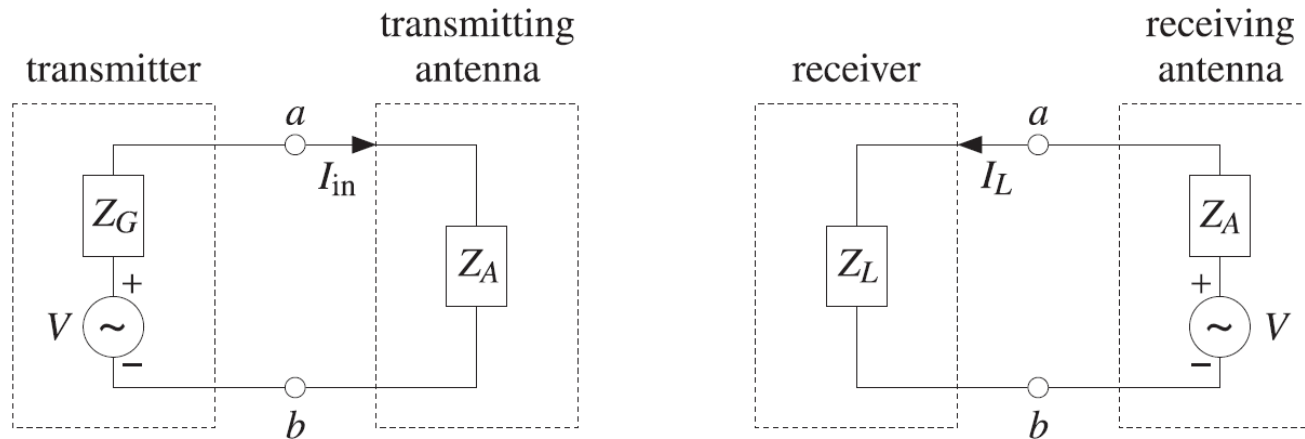


Antennas: Parameters

Impedance

- In Tx and Rx the antenna equivalent circuit of the antenna connected to the transmitter or receiver are:

Kontuz! Antena hartzailea eskuinean dago!!



- In Rx, V is the open circuit voltage of the receiving antenna (V_{CA} circuito abierto in Spanish), as it is the voltage in the antenna terminals when no load is connected.
- V will depend on the E field or power density at the antenna location and on the antenna characteristics.
- If $Z_A \neq Z_L^*$ then some mismatch losses reduce the power at Z_L .

Antennas: Parameters

Impedance

- ❑ The antenna impedance is one of the most important parameters. It indicates if a device can be used as an antenna or not.
- ❑ To measure the impedance normally the network analyzer is used. The impedance can be obtained from the reflection coefficient as follows:

$$\rho = \frac{Z_{in} - Z_0}{Z_{in} + Z_0}$$

Modulia erabiliko dugu gehienetan (edo guztietan).

- ❑ Usually network analyzers provide Z_{in} measurement directly.
- ❑ Other measurements related with ρ and consequently with Z_{in} are:
 - Return losses: $-20\log|\rho|$
 - Voltage Standing Wave Ratio (VSWR) *Relación o Coeficiente de Onda Estacionaria (ROE/COE):*
$$VSWR = \frac{1 + |\rho|}{1 - |\rho|}$$
 - Mismatch Loss: $-10\log[1 - |\rho|^2]$
- ❑ In transmission, a mismatch between the transmitter and the antenna can cause important damage in the equipment due to the reflected power. So good matching is a critical factor.

Ejemplos/adibideak- Transmitting antenna 1


Generator $V_g=30\text{ V}$, $Z_g=50\ \Omega$

a) Power radiated by an antenna with $Z_a=50\ \Omega$

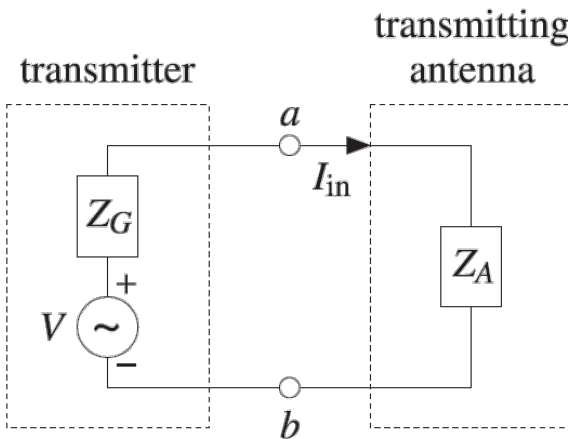b) Power radiated by an antenna with $Z_a=75\ \Omega$

b.1) Mismatch losses (linear units and logarithmic units)

b.2) Reflection coefficient. Mismatch losses (linear and logarithmic)



a) $P_{\text{rad}}|_{Z_a=50} = 4.5\text{ W}$

b) $P_{\text{rad}}|_{Z_a=75} = 4.32\text{ W}$

b.1) Mismatch losses = $P_{\text{rad}}|_{Z_a=75} / P_{\text{rad}}|_{Z_a=50} = 0.96$

Mismatch losses = $10\log_{10}[P_{\text{rad}}|_{Z_a=75} / P_{\text{rad}}|_{Z_a=50}] = -0.177\text{ dB}$

b.2) $\rho=0.2$ $[1-|\rho|^2] = [1-0.2^2] = 0.96$

$10\log[1-|\rho|^2] = 10\log[1-0.2^2] = -0.177\text{ dB}$

The generator can provide 4.5 W to a matched antenna. Due to mismatch, the 75 Ω antenna gets 4.32 W. This suppose -0.177 dB mismatch losses.


Mismatch losses can also be calculated from the reflection coefficient.

Generator nominal power: the power dissipated by a load which impedance is equal to the generator impedance.

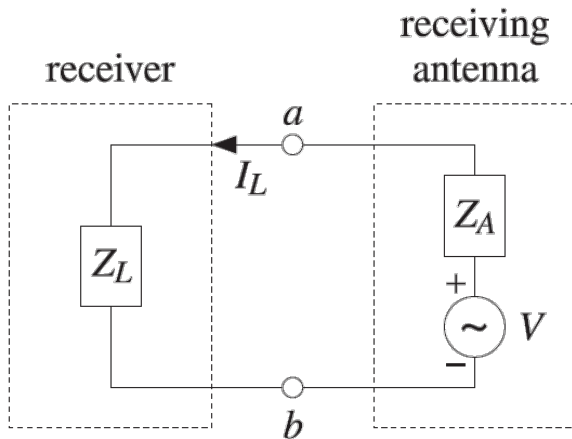Ejemplos/adibideak- Receiving antenna 1

Receiving antenna $Z_A=50 \Omega$. Receiver with $Z_L=75 \Omega$

- Reflection coefficient. Mismatch losses (linear and logarithmic)
- Ratio between power received by the receiver with $Z_L=75 \Omega$ and power received by the antenna ($Z_A=50 \Omega$).
- If the antenna takes 1 mW, how much does the receiver take?



a) $\rho = (75-50)/(75+50) = 0.2$

$$[1 - |\rho|^2] = [1 - 0.2^2] = 0.96$$

$$10 \log [1 - |\rho|^2] = 10 \log [1 - 0.2^2] = -0.177 \text{ dB}$$

b) $P_{\text{receiver}} / P_{\text{antenna}} = \text{mismatch losses} = 0.96$

c) $P_{\text{receiver}} = P_{\text{antenna}} \cdot \text{mismatch losses} = 1 \cdot 0.96 = 0.96 \text{ mW}$

$$P_{\text{receiver}}(\text{dBm}) = P_{\text{antenna}}(\text{dBm}) - \text{mismatch losses}(\text{dB}) = 10 \cdot \log(1) - 0.177 = -0.177 \text{ dBm}$$

The antenna takes 1 mW. Due to impedance mismatch, the 75Ω receiver gets 0.96 mW. This suppose -0.177 dB mismatch losses.

Ejemplos/adibideak- Receiving antenna 2

Receiving antenna $Z_A=50\ \Omega$ taking 1 mW power. How much power would a receiver with $Z_L=100\ \Omega$ take?

Solution:


Reflection coefficient $\rho=(100-50)/(100+50)=1/3$

$$1-|\rho|^2 = 1 - (1/3)^2 = 0.889$$

$$10\log[1-|\rho|^2] = 10\log[1 - (1/3)^2] = -0.51\text{ dB}$$

$$P_{\text{receiver}} = P_{\text{antenna}} \cdot \text{mismatch losses} = 1 \cdot 0.889 = 0.889\text{ mW}$$
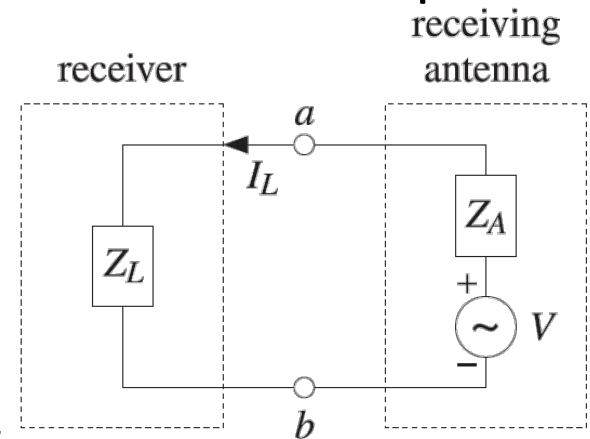
$$P_{\text{receiver}}(\text{dBm}) = P_{\text{antenna}}(\text{dBm}) - \text{mismatch losses}(\text{dB}) = 10 \cdot \log(1) - 0.51 = -0.51\text{ dBm}$$



Matched impedances $Z_L=Z_A=50\ \Omega$, power in $Z_L=1\text{ mW}$, we can calculate V

$$P_{Z_L=50\Omega} = \left| \frac{V}{Z_A + Z_L} \right|^2 \cdot Z_L \Rightarrow V = \sqrt{\frac{P_{Z_L}}{Z_L}} \cdot (Z_A + Z_L) = \sqrt{\frac{10^{-3}}{50}} \cdot (50 + 50) = 0.4472\text{ V}$$

Mismatched impedances $Z_L=100\ \Omega$, $Z_A=50\ \Omega$

$$P_{Z_L=100\Omega} = \left| \frac{V}{Z_A + Z_L} \right|^2 \cdot Z_L = \left| \frac{0.4472}{50 + 100} \right|^2 \cdot 100 = 0.889\text{ mW}$$